

CBSE Question Paper - 2010
DIGITAL ELECTRONICS AND MICRO
PROCESSORS
(Theory) Paper II
Class – XII

Time allowed: 3 hours

Maximum Marks: 60

Instructions: Attempt all questions.

1. (a) What are the applications and advantages of digital signal processing?

4

- (b) Convert the following decimal numbers to binary numbers:

(i) 39

(ii) 185

4

- (c) Add the following binary numbers:

(i) 1001 and 1100

(ii) 1011 and 1111

4

OR

Other Educational Websites:

ICSEGuess.com | NIOSGuess.com | IGNOUGuess.com | IITGuess.com | MagicSense.com | AIPMTGuess.com |
AIEEEGuess.com | IndiaGuess.com

Draw a full adder circuit and explain its operation.

12

2. (a) Explain the following :

4×2

- (i) Priority encoder
- (ii) Seven segment LED display

(b) Give the types of multiplexer and demultiplexer and give one example of each Type.

4

OR

Explain the operation of the following using truth table:

4×3

- (i) RS flip flop
- (ii) D type flip flop
- (iii) JK flip flop

3. (a) Describe the operation of asynchronous counter.

6

(b) Describe the operation of universal shift register.

6

4. Explain the general principle of counter type A/D convertor.

12

OR

(a) Give a brief description of PROM.

6

(b) Explain the expansion of memory in terms of word length and capacity.

6

Other Educational Websites:

ICSEGuess.com | NIOSGuess.com | IGNOUGuess.com | IITGuess.com | MagicSense.com | AIPMTGuess.com | AIEEEGuess.com | IndiaGuess.com

5 (a) Draw the block diagram of 8085 microprocessor.

6

(c) For a microprocessor, explain in brief the following :

6

- (i) Data and address bus
- (ii) Control bus

Other Educational Websites:

ICSEGuess.com | NIOSGuess.com | IGNOUGuess.com | IITGuess.com | MagicSense.com | AIPMTGuess.com |
AIEEEGuess.com | IndiaGuess.com